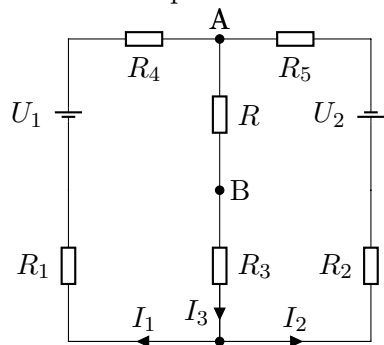


Tema: Zadatak


Nastavni sat predmeta *Osnove elektrotehnike*, listopad 2017.



$$\begin{aligned} U_1 &= 31 \text{ V} & R_3 &= 4 \Omega \\ U_2 &= 4 \text{ V} & R_4 &= 7 \Omega \\ R_1 &= 3 \Omega & R_5 &= 14 \Omega \\ R_2 &= 6 \Omega & U_{AB} &= 6 \text{ V} \end{aligned}$$

$$R = ?$$

K1K2b.1

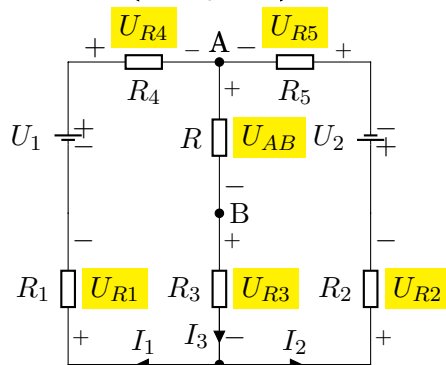

$$\begin{aligned} I_3 &= I_1 + I_2 & (1) \\ U_{R1} - U_1 + U_{R4} + U_{AB} + U_{R3} &= 0 & (2) \\ U_{R2} + U_2 + U_{R5} + U_{AB} + U_{R3} &= 0 & (3) \end{aligned}$$

$$U_{R1} = I_1 R_1, U_{R2} = I_2 R_2, U_{R3} = I_3 R_3, U_{R4} = I_1 R_4, U_{R5} = I_2 R_5$$

$$I_1 + I_2 - I_3 = 0 \quad (1)$$

$$I_1 R_1 + I_1 R_4 + I_3 R_3 = U_1 - U_{AB} \quad (2)$$

$$I_2 R_2 + I_2 R_5 + I_3 R_3 = -U_2 - U_{AB} \quad (3)$$

K1K2b.2

$$I_1 \quad \quad \quad + I_2 \quad \quad \quad - I_3 \quad \quad \quad = 0 \quad (1)$$

$$I_1(3 + 7) \quad \quad \quad \quad \quad \quad \quad \quad \quad \quad \quad + I_3 \cdot 4 \quad \quad \quad = 31 - 6 \quad (2)$$

$$\quad + I_3 \cdot 4 \quad \quad \quad = -4 - 6 \quad (3)$$

$$I_1 \quad \quad \quad + I_2 \quad \quad \quad - I_3 \quad \quad \quad = 0 \quad (1)$$

$$10I_1 \quad + 4I_3 \quad \quad \quad = 25 \quad (2)$$

$$\quad + 4I_3 \quad \quad \quad = -10 \quad (3)$$

Rješenje sustava: $I_1 = 2 \text{ A}, I_2 = -0,75 \text{ A}, I_3 = 1,25 \text{ A}$

$$R = \frac{U_{AB}}{I_3} = \frac{6}{1,25} = 4,8 \Omega$$

K1K2b.3